
DAY 13
MEMORY ELEMENTS - III

October 30, 2023

SRAM Controller

Test Procedures

1. Initialization:
Reset (rstn) is asserted low, and all control signals are initialized. The clock is set to 0.
2. Reset De-assertion:
After 1 time unit, rstn is de-asserted to initiate the operation of the SRAM.
3. Test Case 1 - Writing to SRAM:
Write 24 to address 28.
4. Test Case 2 - Reading from SRAM:
Read from address 28, expecting to retrieve 24.
5. Test Case 3 - Writing to SRAM:
Write 30 to address 28.
6. Test Case 4 - Reading from SRAM:
Read from address 28, expecting to retrieve 24 (since previous write should not have taken effect due to the lack of a write enable signal).
7. Test Case 5 - Reading from SRAM:
Read from address 28, expecting to retrieve 24.
8. Termination:
After 5 time units, the simulation is finished.

SRAM Controller Module

```
module sram_tb;

reg clk,rstn;
reg CS_b, WE_b, OE_b;
reg [10:0] addr;
wire [15:0] data_read;
reg [15:0] data_write;

wire [15:0] data;

assign data = ((CS_b == 0) && (WE_b == 0) && (OE_b == 1)) ? data_write :
'bz;
assign data_read = ((CS_b == 0) && (WE_b == 1) && (OE_b == 0)) ? data :
'bz;

sram INST0 (.clk(clk),.rstn(rstn),.CS_b(CS_b),.WE_b(WE_b),.OE_b(OE_b),
            .addr(addr),.data(data_read));

always begin
    #1 clk = ~clk;
end

initial begin
    $dumpfile("sram_sim.vcd");
    $dumpvars(0,sram_tb);
    CS_b = 1;
    WE_b = 0;
    data_write =0;
    OE_b =0;
    addr=0;

    clk = 0;
    rstn = 0;
    #1
    rstn = 1;

    // TestCase: Writing to SRAM.
    #1
```

```
        OE_b = 1;
        CS_b = 0;
        WE_b = 0;
        data_write = 24;
        addr = 28;

        // // TestCase: Reading the sram.
        #2
        OE_b = 0;
        CS_b = 0;
        WE_b = 1;
        data_write = 26;
        addr = 28;

        // TestCase: Writing to memory location 28;
        #1
        OE_b = 1;
        CS_b = 0;
        WE_b = 0;
        data_write = 30;
        addr = 28;

        // TestCase: Memory location 28 should be the same as before.
        #1
        OE_b = 0;
        CS_b = 0;
        WE_b = 1;
        data_write = 40;
        addr = 28;

        // TestCase: Memory location 28 should be the same as before.
        #1
        OE_b = 0;
        CS_b = 0;
        WE_b = 1;
        data_write = 40;
        addr = 28;

        #5
        $finish;

    end
endmodule
```

Simulation

 


Figure 1: Simulation Results